#### 1

## ASSEMBLY ASSIGNMENT

### CHAKALI SURESH

# chakalisuresh2223@gmail.com

## IITH - IITH-Future Wireless Communication

#### **CONTENTS**

#### III. LOGIC DIAGRAM

I	Question	1	
II	Answer	1 X —	
III	Logic Diagram	1	
IV	Truth Table	1 Y —	
$\mathbf{V}$	K-Map Implementation	1	
VI	Components	2 Z—	
VII	Implementation	2	Fig. 1

### I. QUESTION

A Boolean function F of three X, Y and Z is given as  $F(X,Y,Z)=(X'+Y+Z)\cdot(X+Y'+Z')\cdot(X'Y+Z')\cdot(X'Y'Z'+X'YZ'+XYZ')$ . Which one of the following is true?

(a) 
$$F(X,Y,Z) = (X+Y+Z') \cdot (X'+Y'+Z')$$
  
(b)  $F(X,Y,Z) = (Y'+Y) \cdot (Y+Y'+Z')$ 

(b) 
$$F(X, Y, Z) = (X' + Y) \cdot (X + Y' + Z')$$

(c) 
$$F(X, Y, Z) = X'Z' + YZ'$$

 $(X'+Y)\cdot Z'$ 

(d) 
$$F(X,Y,Z) = X'Y'Z + XYZ$$

#### II. ANSWER

#### IV. TRUTH TABLE

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Truth table for Boolean Function F

### V. K-MAP IMPLEMENTATION

Using the boolean logic output F can be expressed in terms of the inputs X, Y, Z with the help of the following Kmap.

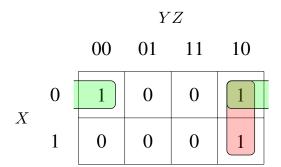


Fig. 2

## VI. COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
LED		1
Resistor	220ohms	1
Jumper	M-M	5
Wires		
Breadboard		1

VII. IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	X	
3	Y	
4	Z	
13		F

Connections

## **Procedure**

- 1. Connect the circuit as per the above table.
- 2. Connect inputs to Vcc for logic 1, ground for logic 0.
- 3. Execute the circuit using the below code.

https://github.com/Chakali23/FWC/tree/main/	
IDE/Assembly	

4. Change the values of X,Y,Z in the code and verify the Truth Table.