

# ASSEMBLY ASSIGNMENT

Chakali Suresh

chakalisuresh2223@gmail.com

IITH - Future Wireless Communication

## CONTENTS


<b>I</b>	<b>Question</b>	1
<b>II</b>	<b>Answer</b>	1
	II-A Truth Table . . . . .	1
	II-B K-Map Implementation . . . . .	1
<b>III</b>	<b>Components</b>	2
<b>IV</b>	<b>Implementation</b>	2

### B. K-Map Implentation

		$Q_1 Q_2$			
		00	01	11	10
$Q_0$	0	1	0	0	0
	1	1	0	0	0

## I. QUESTION

The digital circuit shown \_\_\_\_\_

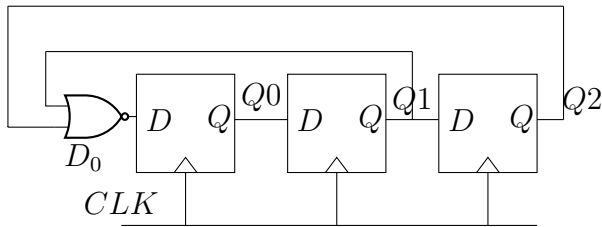

$$D_0 = \overline{Q_1} + \overline{Q_2}$$

		$Q_1 Q_2$			
		00	01	11	10
$Q_0$	0	0	0	0	0
	1	1	0	0	1

## II. ANSWER

The above question can be solved by using Truth Table and karnaugh-map.

### A. Truth Table

Present State			Flip-Flop i/p			Next State		
$Q_0$	$Q_1$	$Q_2$	$D_0$	$D_1$	$D_2$	$Q'_0$	$Q'_1$	$Q'_2$
0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	1	1	0
1	1	0	0	1	1	0	1	1
0	1	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

$$D_1 = Q_0$$

		$Q_1 Q_2$			
		00	01	11	10
$Q_0$	0	0	0	1	0
	1	0	0	0	1

$$D_2 = Q_1$$

Therefore, given circuit is Divide by 5 circuit.

### III. COMPONENTS

Components	Values	Quantity
VAMAN		1
Jumper Wires	M-M	25
Breadboard		1
LED		4
Resistor		
Flip Flop	7474	2

### IV. IMPLEMENTATION

	INPUT			OUTPUT			CLOCK		5V			
	Q0	Q1	Q2	Q0'	Q1'	Q2'						
VAMAN(pins)	2	3	4	18	21	22	5					
7474	5	9		2	12		CLK1	CLK2	1	4	10	13
7474			9			12	CLK1	CLK2	1	4	10	13

Connections

#### Procedure

1. Connect the circuit as per the above table.
2. Connect LEDs to the output pins of the VAMAN to see output.
3. Execute the circuit using the below code.

[https://github.com/Chakali23/FWC/tree/main/IDE/arm\(VAMAN\)](https://github.com/Chakali23/FWC/tree/main/IDE/arm(VAMAN))