

IOT ASSIGNMENT


Chakali Suresh
chakalisuresh2223@gmail.com
IITH - Future Wireless Communication

CONTENTS

I	Question	1
II	Answer	1
III	K-Map Implementation	1
IV	Truth Table	1
V	Logic Diagram	1
VI	Components	1
VII	Implementation	1

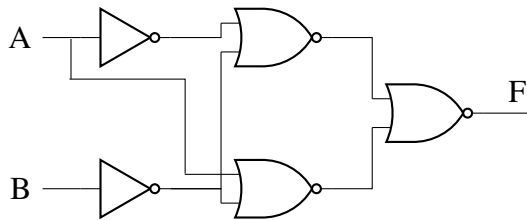I. QUESTION

The logic block shown has an output F given by _____



- (A) $A + B$
(B) $A \cdot \bar{B}$

- (C) $A + \bar{B}$
(D) \bar{B}

II. ANSWER

The above question can be solved as follows:
 $\rightarrow \bar{A} \cdot \bar{B} + A \cdot \bar{B}$
 $\rightarrow (A + \bar{A}) \cdot \bar{B}$
 $\rightarrow \bar{B}$
 Therefore, the output $F = \bar{B}$.

III. K-MAP IMPLEMENTATION

		B	
		0	1
A	0	1	0
	1	1	0

Therefore $F = \bar{B}$.

IV. TRUTH TABLE

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

Truth table for Boolean function F

V. LOGIC DIAGRAM

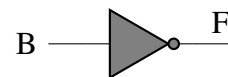


Fig. 2

VI. COMPONENTS

Components	Values	Quantity
VAMAN		1
Jumper Wires	M-M	4
Breadboard		1

VII. IMPLEMENTATION

VAMAN PIN	INPUT	OUTPUT
2	A	
4	B	
13		F

Connections

Procedure

1. Connect the circuit as per the above table.
2. Connect inputs to Vcc for Logic 1 and ground for Logic 0.
3. Execute the circuit using the provided codes.

Approach 1

[https://github.com/Chakali23/FWC/tree
/main/IDE/IOT](https://github.com/Chakali23/FWC/tree/main/IDE/IOT)

4. Change the values of A and B in the hardware and verify the truth table.