

FPGA ASSIGNMENT

Chakali Suresh


chakalisuresh2223@gmail.com

IITH - Future Wireless Communication

CONTENTS

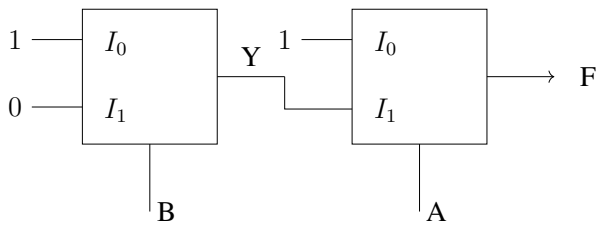I. QUESTION

The output F of the digital circuit shown can be written in form(s) _____



- (a) $\overline{A} \cdot \overline{B}$
- (b) $\overline{A} + \overline{B}$
- (c) $\overline{A} + B$
- (d) $\overline{A} \cdot B$

II. ANSWER

The above question can be reduced as follows
 $\rightarrow Y = \overline{B} \cdot 1 + B \cdot 0 \rightarrow Y = \overline{B}$
 $\rightarrow F = \overline{A} \cdot 1 + A \cdot \overline{B} \rightarrow F = (\overline{A} + A) \cdot (\overline{A} + \overline{B})$
 $\rightarrow F = \overline{A} + \overline{B}$ also $F = \overline{A \cdot B}$
 Therefore, the Boolean function $F = \overline{A} + \overline{B}$

III. LOGIC DIAGRAM

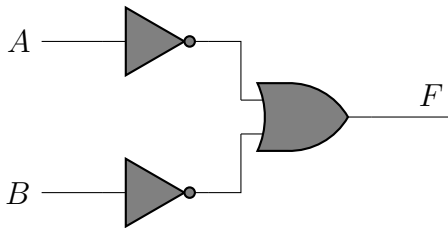


Fig. 1

IV. TRUTH TABLE

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Truth table for Boolean Function F

V. K-MAP IMPLEMENTATION

Using the boolean logic output F can be expressed in terms of the inputs A, B with the help of the following K-map.

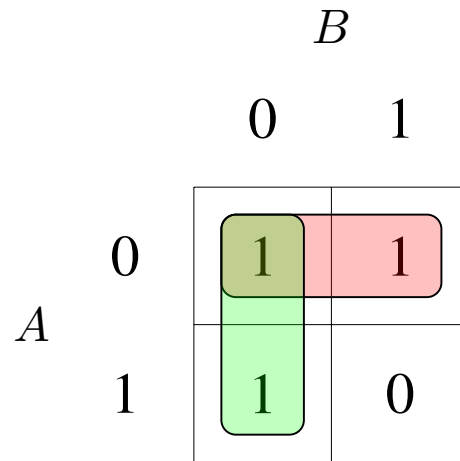


Fig. 2

VI. COMPONENTS

Component	Values	Quantity
VAMAN		1
LED		1
Jumper Wires	M-M	4
Breadboard		1

VII. IMPLEMENTATION

VAMAN IOpins	INPUT	OUTPUT
5	A	
6	B	
2		F

Connections

Procedure

1. Connect the circuit as per the above table.
2. Connect inputs to Vcc for logic 1, ground for logic 0.
3. Execute the circuit using the below code.

https://github.com/Chakali23/FWC/ tree/main/IDE/fpga(VAMAN)
--

4. Change the values of A,B in the hardware and verify the Truth Table.